

LAB 1

IMPLEMENTATION OF BASIC COMBINATION LOGIC CIRCUIT USING VERILOG

Phạm Quang Vinh ITITIU21347


II.1 LAB EXPERIMENT 1 : WRITE HDL CODE TO REALIZE ALL LOGIC GATES

// data flow

```
module lab1_ex1(SW,LEDG,LEDR);
    input[17:0] SW;
    output[7:0] LEDG;
    output[17:0] LEDR;
    assign LEDR=SW;
    allgate_DF
DUT(.a(SW[1]),.b(SW[0]),.yand(LEDG[6]),.yor(LEDG[5]),.ynot(LEDG[4]),.ynand(LEDG[3]),.ynor(LEDG[2]),.yxor(LEDG[1]),.yxnor(LEDG[0]));
endmodule
```

```
module allgate_DF ( a, b, yand,yor,ynot,ynand,ynor,yxor,yxnor );
```


```
input a,b;
    output yand, yor, ynot, ynand, ynor, yxor, yxnor;
    assign yand = a & b;           // AND Operation
    assign yor = a | b;           // OR Operation
    assign ynot = ~a;             // NOT Operation
    assign ynand = ~(a & b);      // NAND Operation
    assign ynor = ~(a | b);       //NOR Operation
    assign yxor = a ^ b;          //XOR Operation
    assign yxnor = ~(a^b);        //XNOR Operation
endmodule
```

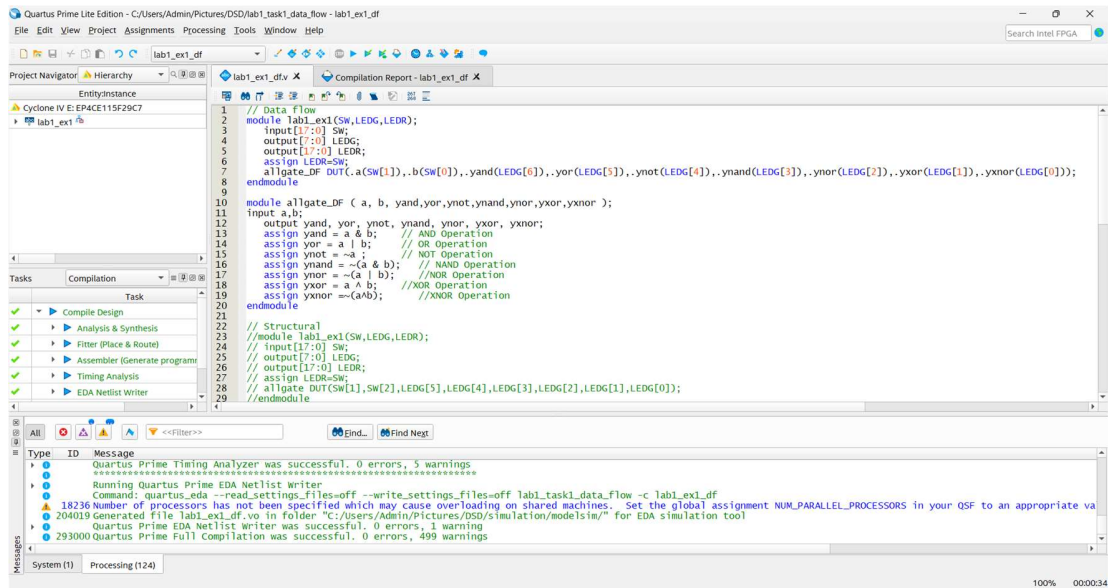

// Structural


```
module lab1_ex1(SW,LEDG,LEDR);
    input[17:0] SW;
    output[7:0] LEDG;
    output[17:0] LEDR;
    assign LEDR=SW;
    allgate DUT(SW[1],SW[2],LEDG[5],LEDG[4],LEDG[3],LEDG[2],LEDG[1],LEDG[0]);
endmodule
```

```
module allgate ( a, b, yand,yor,ynot,ynand,ynor,yxor,yxnor );
    input a,b;
    output yand, yor, ynot, ynand, ynor, yxor, yxnor;
    assign yand = a & b;           // AND Operation
    assign yor = a | b;           // OR Operation
    assign ynot = ~a;             // NOT Operation
    assign ynand = ~(a & b);      // NAND Operation
    assign ynor = ~(a | b);       //NOR Operation
    assign yxor = a ^ b;          //XOR Operation
    assign yxnor =~(a^b);         //XNOR Operation
endmodule
```

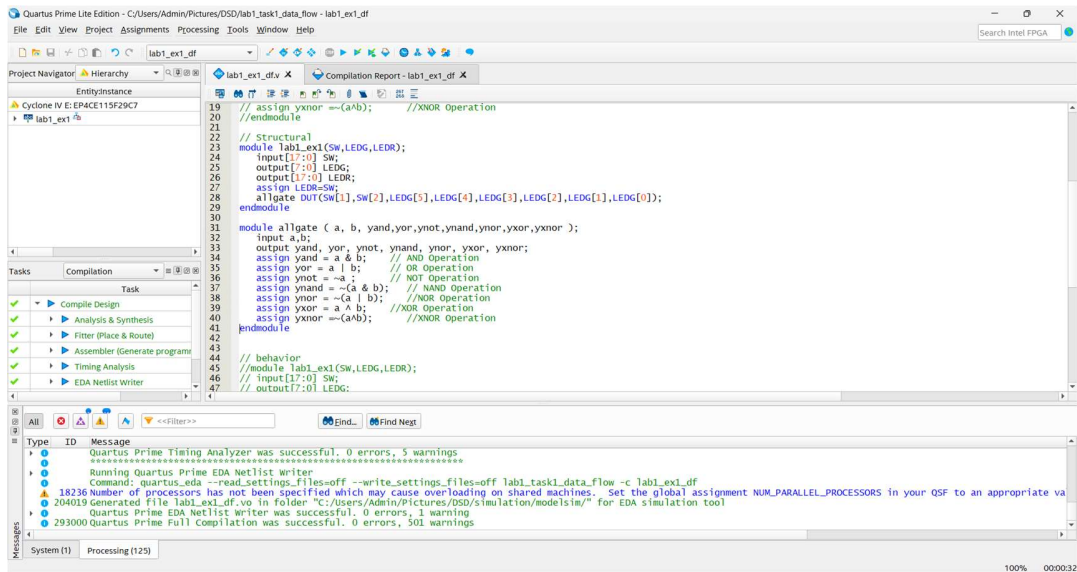

```
// behavior
module lab1_ex1(SW,LEDG,LEDR);
    input[17:0] SW;
    output[7:0] LEDG;
    output[17:0] LEDR;
    assign LEDR=SW;
    allgate_BH DUT(SW[1],SW[2],LEDG[5],LEDG[4],LEDG[3],LEDG[2],LEDG[1],LEDG[0]);
endmodule

module allgate_BH ( a, b, yand,yor,ynot,ynand,ynor,yxor,yxnor );
    input a,b;
    output yand, yor, ynot, ynand, ynor, yxor, yxnor;
    reg yand, yor, ynot, ynand, ynor, yxor, yxnor;
    always @(*)
    begin
        yand = a & b;           // AND Operation
        yor = a | b;           // OR Operation
        ynot = ~a ;           // NOT Operation
        ynand = ~(a & b);      // NAND Operation
        ynor = ~(a | b);       //NOR Operation
        yxor = a ^ b;          //XOR Operation
        yxnor =~(a^b);         //XNOR Operation
    end
endmodule
```

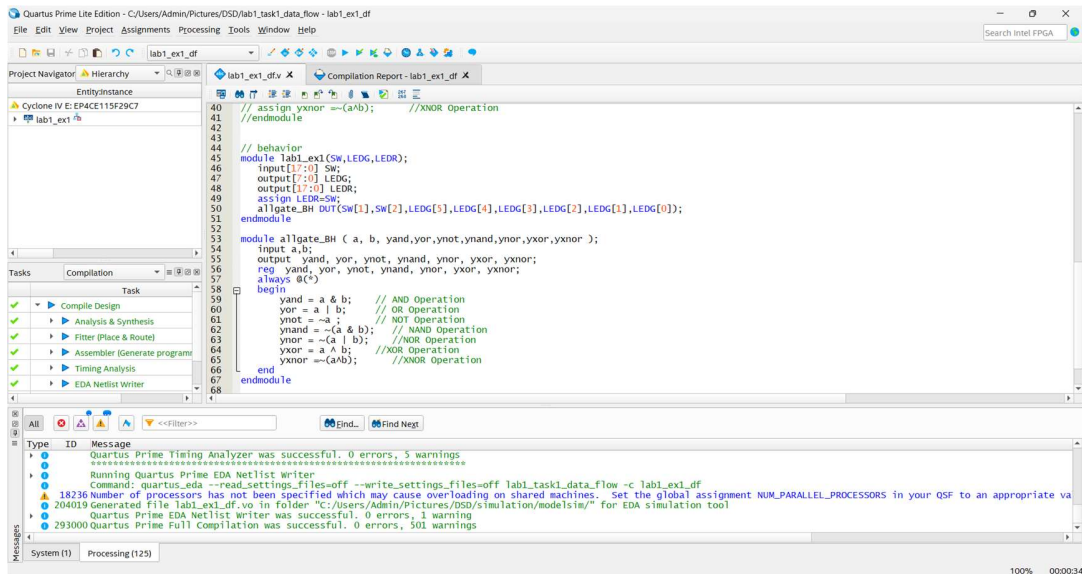

II.2 LAB EXPERIMENT 2 : WRITE VERILOG HDL CODES TO SIMULATE AND IMPLEMENT THE HALF ADDER CIRCUIT:

// Structural

```


module Lab1_task2_STRUC(SW,LEDR,LEDG);
    input[0:17] SW;
    output[0:7] LEDR;
    output[0:17] LEDG;
    assign LEDG=SW;
    half_adder_structural DUT(.a(SW[0]),.b(SW[1]),.s(LEDR[0]),.Cout(LEDR[1]));
endmodule

```

```

module half_adder_structural(input a, b, output s, Cout);
    xor G1(s,a,b);
    and G2(Cout,a,b);
endmodule


```

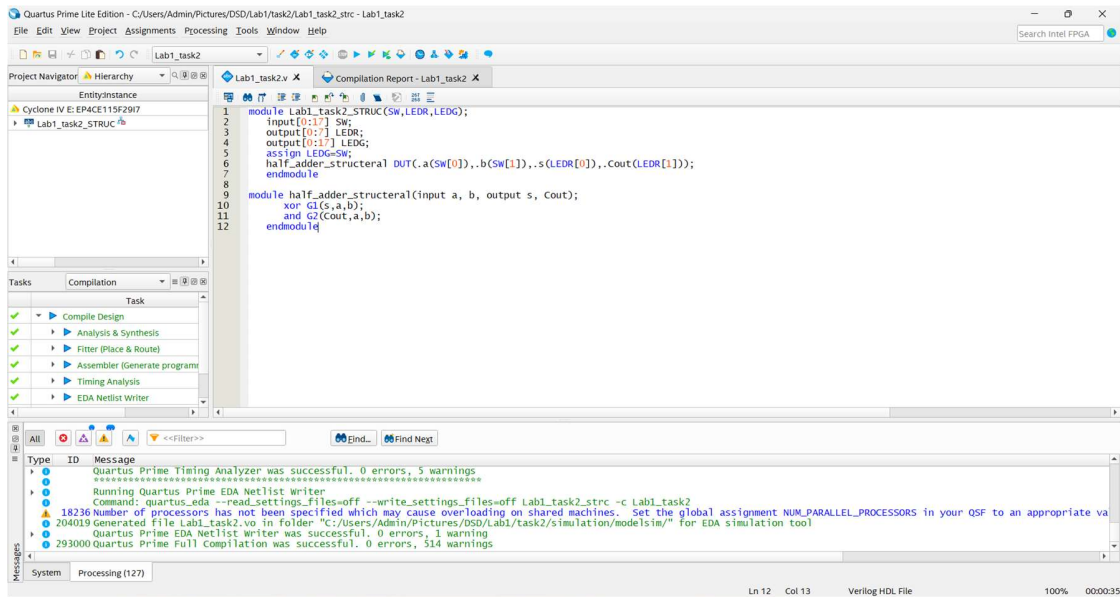

// data flow

```
module Lab1_task2(SW,LEDR,LEDG);
    input[0:17] SW;
    output[0:7] LEDR;
    output[0:17] LEDG;
    assign LEDG=SW;
    half_adder_dataflow DUT(.a(SW[0]),.b(SW[1]),.s(LEDR[0]),.Cout(LEDR[1]));
endmodule
```

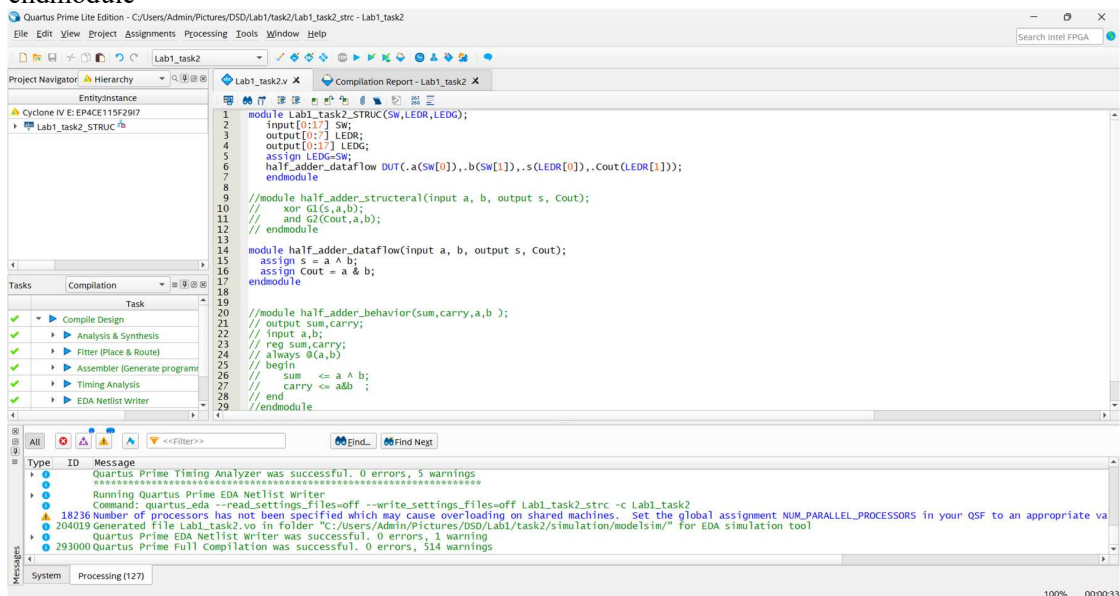
```
module half_adder_dataflow(input a, b, output s, Cout);
    assign s = a ^ b;
    assign Cout = a & b;
endmodule
```



// Behavior

```
module Lab1_task2(SW,LEDR,LEDG);
    input[0:17] SW;
    output[0:7] LEDR;
    output[0:17] LEDG;
    assign LEDG=SW;
    half_adder_behavior DUT(.a(SW[0]),.b(SW[1]),.sum(LEDR[0]),.carry(LEDR[1]));
endmodule
```
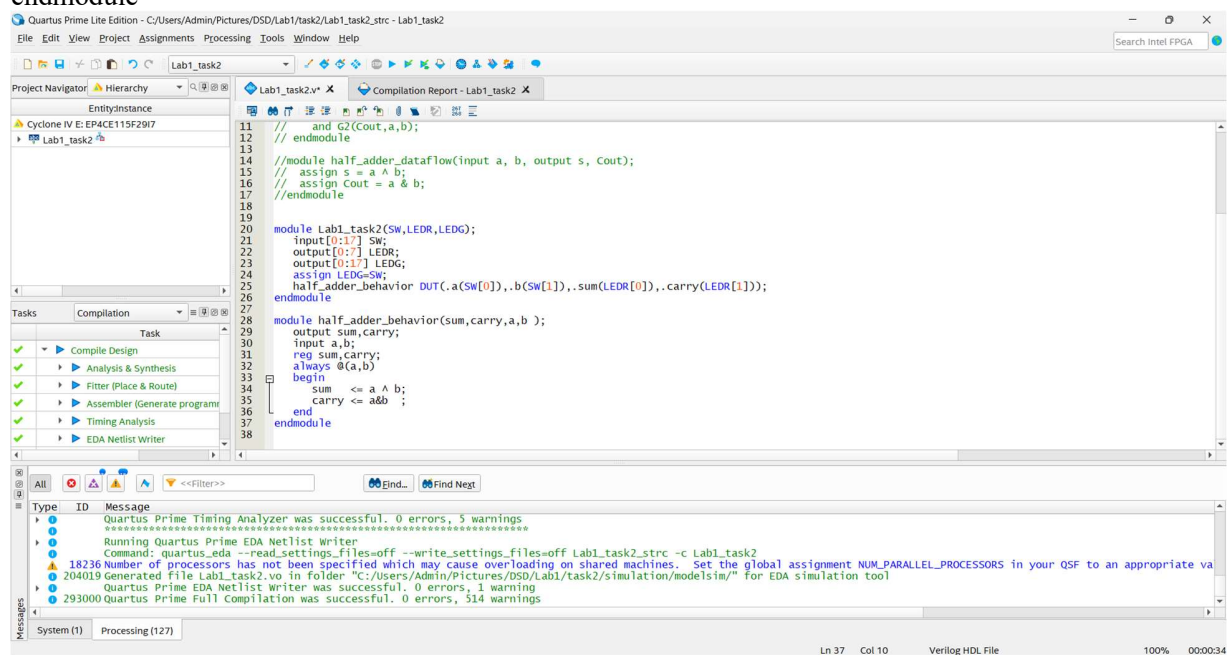
```
module half_adder_behavior(sum,carry,a,b );
    output sum,carry;
    input a,b;
    reg sum,carry;
    always @(a,b)
    begin
        sum <= a ^ b;
        carry <= a&b ;
    end
endmodule
```






II.3 EXPERIMENT 3: WRITE VERILOG HDL CODES TO SIMULATE AND IMPLEMENT THE FULL ADDER CIRCUIT:

```
// dataflow
module Lab1_task3(SW,LEDG,LEDR);
    input[17:0] SW;
    output[7:0] LEDG;
    output[17:0] LEDR;
    assign LEDR= SW;
    full_adder_DTFL DUT(SW[2],SW[1],SW[0],LEDG[1],LEDG[0]);
endmodule


module full_adder_DTFL(input a, b, c, output Sum, Cout);
    assign Sum= a ^ b ^ c;
    assign Cout= (a&b)|(b&c)|(a&c);
endmodule
```

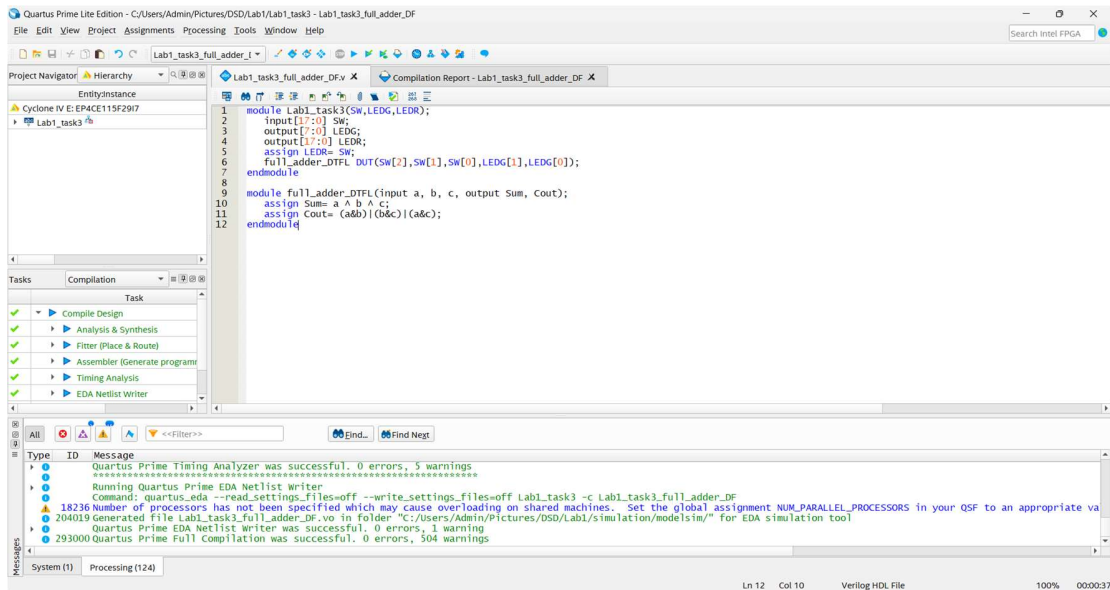

// Structural

```
module Lab1_task3(SW,LEDG,LEDR);
    input[17:0] SW;
    output[7:0] LEDG;
    output[17:0] LEDR;
    assign LEDR= SW;
    full_adder_STRU DUT(SW[2],SW[1],SW[0],LEDG[1],LEDG[0]);
endmodule
```


```
module full_adder_STRU(A,B,Cin,Sum,Carry);
    output Sum,Carry;
    input A,B,Cin;
    wire x,y,z;
    xor g1(x,A,B);
    xor g2(Sum,x,Cin);
    and g3(y,x,Cin);
    and g4(z,A,B);
    or g5(Carry,x,y);
endmodule
```

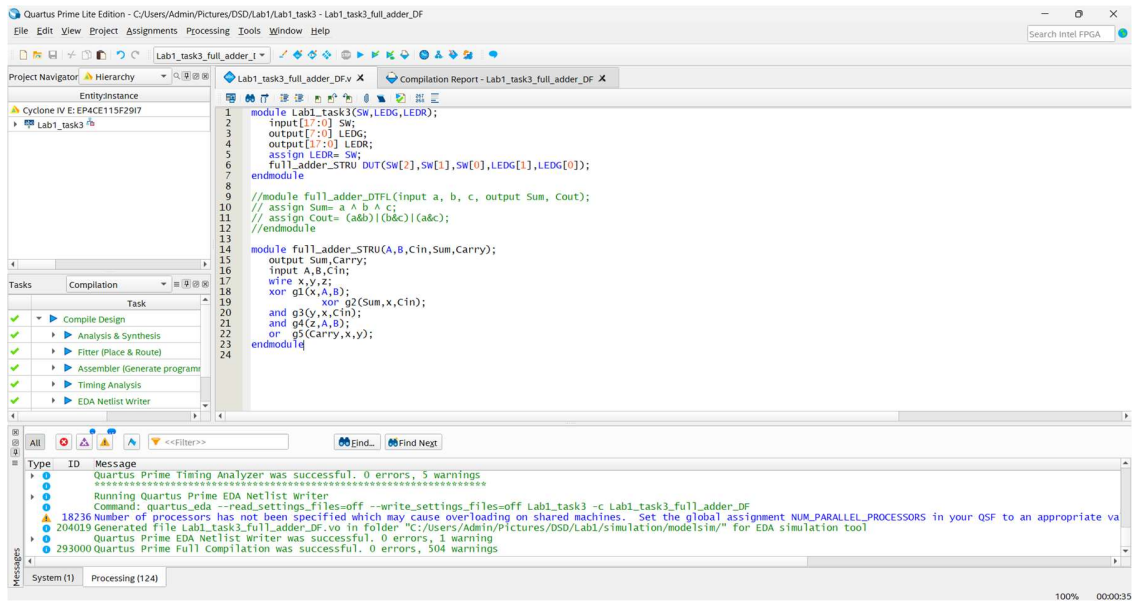// Behavior

```
module Lab1_task3(SW,LEDG,LEDR);
    input[17:0] SW;
    output[7:0] LEDG;
    output[17:0] LEDR;
    assign LEDR= SW;
    full_adder_BH DUT(SW[2],SW[1],SW[0],LEDG[1],LEDG[0]);
endmodule
```

```
module full_adder_BH(a,b,c,sum,carry);
    output sum,carry;
    input a,b,c;
    reg sum,carry;
    always @ (a,b,c)
        begin
            sum <= a^ b^c;
            carry <=(a&b) | (b&c) | (c&a);
        end
endmodule
```

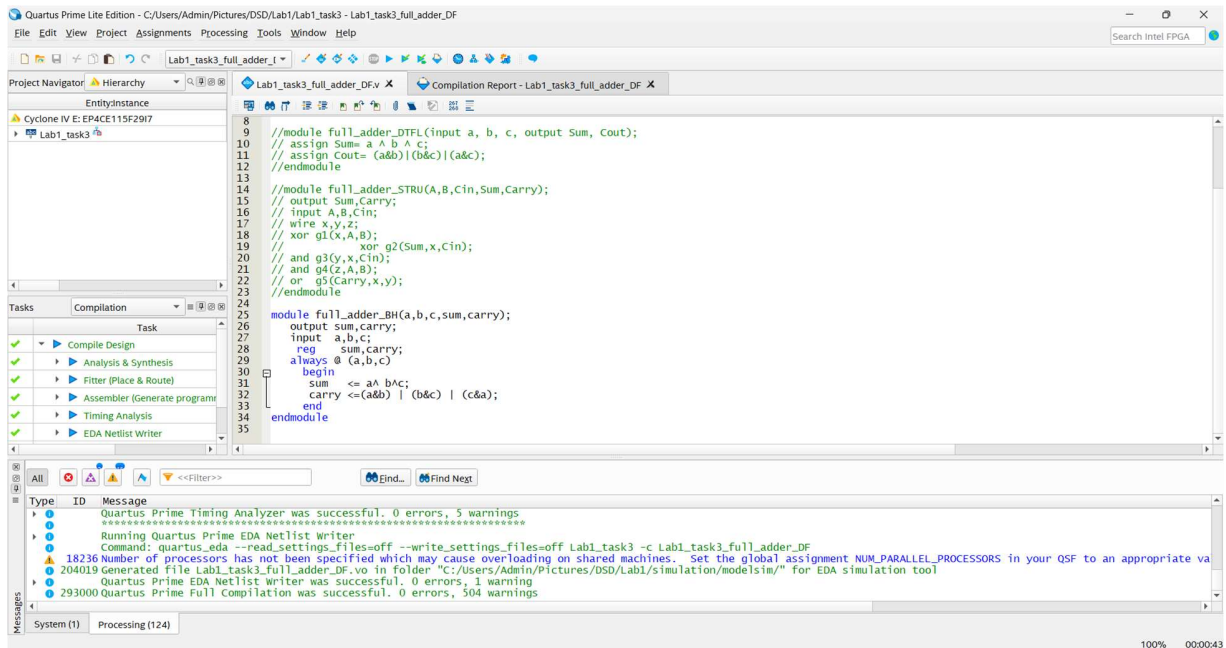

```

module Lab1_task3(SW,LEDG,LEDR);
    input[17:0] SW;
    output[7:0] LEDG;
    output[17:0] LEDR;
    assign LEDR= SW;
    full_adder DUT(SW[2],SW[1],SW[0],LEDG[1],LEDG[0]);
endmodule

```

```

module full_adder( A, B, Cin, S, Cout);
    input wire A, B, Cin;
    output reg S, Cout;

    always @(A or B or Cin)
    begin
        if(A==0 && B==0 && Cin==0)
        begin
            S=0;
            Cout=0;
        end

        else if(A==0 && B==0 && Cin==1)
        begin
            S=1;
            Cout=0;
        end

        else if(A==0 && B==1 && Cin==0)
        begin
            S=1;
            Cout=0;
        end
    end
endmodule

```

```

else if(A==0 && B==1 && Cin==1)
begin
    S=0;
    Cout=1;
end

else if(A==1 && B==0 && Cin==0)
begin
    S=1;
    Cout=0;
end

else if(A==1 && B==0 && Cin==1)
begin
    S=0;
    Cout=1;
end


else if(A==1 && B==1 && Cin==0)
begin
    S=0;
    Cout=1;
end


else if(A==1 && B==1 && Cin==1)
begin
    S=1;
    Cout=1;
end

end

endmodule

```

 

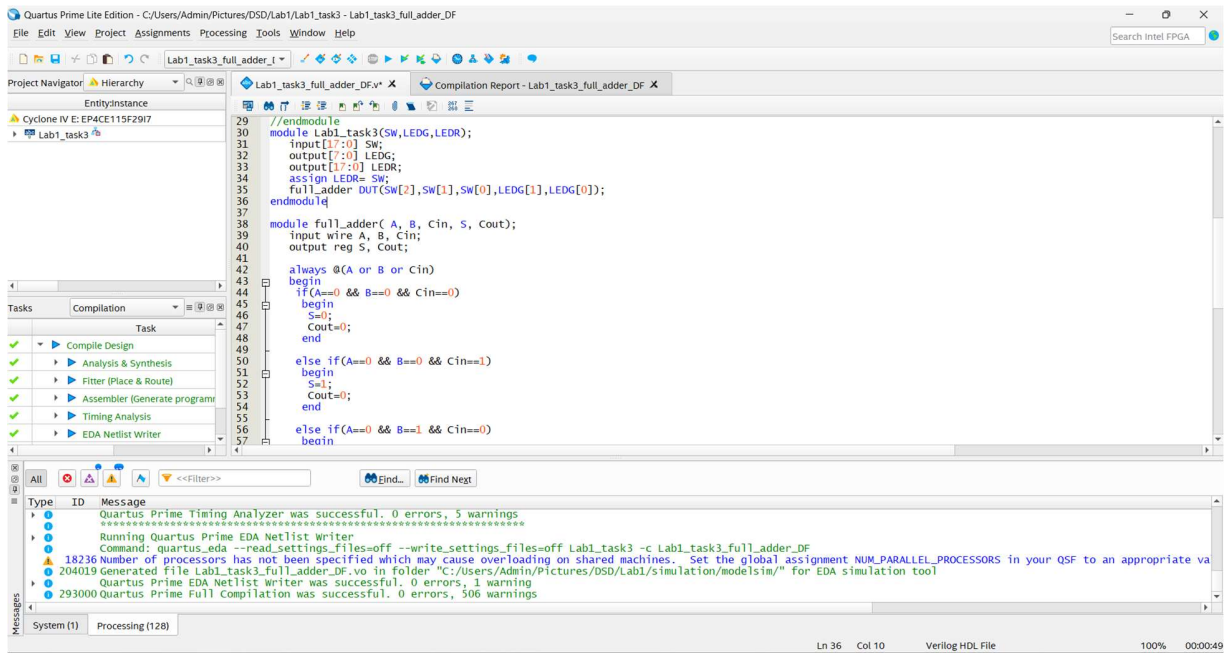

EXTRA

```
module Lab1_extra_1(SW,LEDR,LEDG);
```

```
  input [17:0] SW;
```

```
  output [17:0] LEDR;
```

```
  output [0:7] LEDG;
```

```
  assign LEDR=SW;
```

```
  mux81str
```

```
  DUT(.i0(SW[0]),.i1(SW[1]),.i2(SW[2]),.i3(SW[3]),.i4(SW[4]),.i5(SW[5]),.i6(SW[6]),.i7(SW[7]),.s0(SW[8]),.s1(SW[9]),.s2(SW[10]),.y(LEDG[0]));
endmodule
```

```
module mux81str(i0,i1,i2,i3,i4,i5,i6,i7,s0,s1,s2,y);
```

```
  input i0,i1,i2,i3,i4,i5,i6,i7,s0,s1,s2;
```

```
  output y;
```

```
  wire a,b,c,d,e,f,g,h,n_s0,n_s1,n_s2;
```

```
  not N0(n_s0,s0);
```

```
  not N1(n_s1,s1);
```

```
  not N2(n_s2,s2);
```

```
  and G0(a,i0, n_s2, n_s1, n_s0);
```

```
  and G1(b,i1, n_s2, n_s1, s0);
```

```
  and G2(c,i2, n_s2, s1, n_s0);
```

```
  and G3(d,i3, n_s2, s1, s0);
```

```
  and G4(e,i4, s2, n_s1, n_s0);
```


```
  and G5(f,i5, s2, n_s1, s0);
```

```
  and G6(g,i6, s2, s1, n_s0);
```

```
  and G7(h,i7, s2, s1, s0);
```

```
  or G8(y,a,b,c,d,e,f,g,h);
```

```
endmodule
```

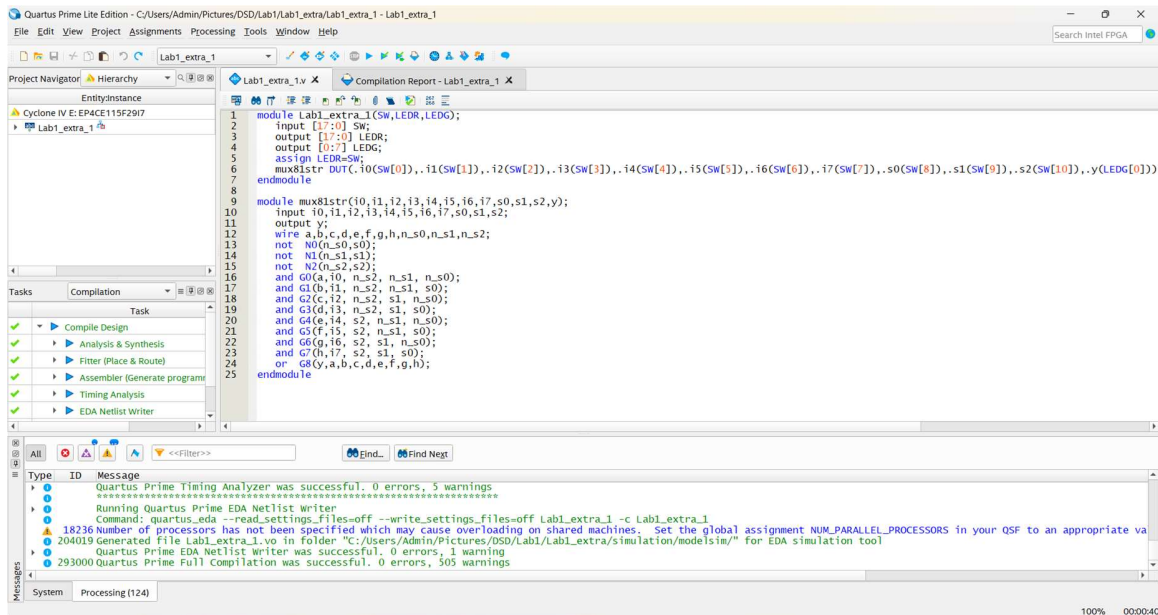

Extra 1a

```

module lab1_extra_ex1a(SW,LEDR,LEDG);
    input [17:0] SW;
    output [17:0] LEDR;
    output LEDG;
    assign LEDR=SW;
    modulemux81str DUT(.i(S[10:3]),.s(SW[2:0]).y(LEDG[0]));
endmodule

```

```

modulemux81str(i,s,y);
input [7:0] i;
input [2:0] s;
output y;
wire [7:0] out_and;
wire [2:0] n_s;
;
not N0(n_s[0],s[0]);
not N1(n_s[1],s[1]);
not N2(n_s[2],s[2]);

```

```

and G0(out_and[0],i[0], n_s[2], n_s[1], n_s[0]);
and G1(out_and[1],i[1], n_s[2], n_s[1], s[0]);
and G2(out_and[2],i[2], n_s[2], s[1], n_s[0]);
and G3(out_and[3],i[3], n_s[2], s[1], s[0]);
and G4(out_and[4],i[4], s[2], n_s[1], n_s[0]);
and G5(out_and[5],i[5], s[2], n_s[1], s[0]);
and G6(out_and[6],i[6], s[2], s[1], n_s[0]);
and G7(out_and[7],i[7], s[2], s[1], s[0]);
or G8(y,out_and[7:0]);

```

endmodule

Quartus Prime Lite Edition - C:/Users/Admin/Pictures/OSD/Lab1/lab1_extra_1_a/lab1_extra_1_a - lab1_extra_1_a

File Edit View Project Assignments Processing Tools Window Help

lab1_extra_1_a

Project Navigator Hierarchy

Entity/Instance

Cyclone IV E: EP4CE115F29C7

lab1_extra_1_a

```
1 module Lab1_extra_1_a(SW,LEDR,LEDG);
2   input [7:0] SW;
3   output [7:0] LEDR;
4   output [7:0] LEDG;
5   assign LEDR=SW;
6   mux81str DUT(.i(SW[10:3]),.s(SW[2:0]),.y(LEDG[0]));
7 endmodule
8
9 module mux81str(i,s,y);
10  input [7:0] i;
11  input [2:0] s;
12  output y;
13  wire [7:0] out_and;
14  wire [2:0] n_s;
15
16  not N0(n_s[0],s[0]);
17  not N1(n_s[1],s[1]);
18  not N2(n_s[2],s[2]);
19
20  and G0(out_and[0],i[0], n_s[2], n_s[1], n_s[0]);
21  and G1(out_and[1],i[1], n_s[2], n_s[1], s[0]);
22  and G2(out_and[2],i[2], n_s[2], s[1], n_s[0]);
23  and G3(out_and[3],i[3], n_s[2], s[1], s[0]);
24  and G4(out_and[4],i[4], s[2], n_s[1], n_s[0]);
25  and G5(out_and[5],i[5], s[2], n_s[1], s[0]);
26  and G6(out_and[6],i[6], s[2], s[1], n_s[0]);
27  and G7(out_and[7],i[7], s[2], s[1], s[0]);
28  or s8(y,out_and[7:0]);
29 endmodule
```

Tasks

Compilation

Task

- Compile Design
- Analysis & Synthesis
- Fitter (Place & Route)
- Assembler (Generate program)
- Timing Analysis
- EDA Netlist Writer

Messages

System Processing (127)

Quartus Prime Timing Analyzer was successful. 0 errors, 5 warnings

Running Quartus Prime EDA Netlist Writer

Command: quartus_eda --read_settings_files=off --write_settings_files=off lab1_extra_1_a -c lab1_extra_1_a

18236 Number of processors has not been specified which may cause overloading on shared machines. Set the global assignment NUM_PARALLEL_PROCESSORS in your QSF to an appropriate value

204019 Generated file lab1_extra_1_a.vo in folder "C:/Users/Admin/Pictures/OSD/Lab1/lab1_extra_1_a/simulation/modelsim/" for EDA simulation tool

Quartus Prime EDA Netlist Writer was successful. 0 errors, 1 warning

293000 Quartus Prime Full Compilation was successful. 0 errors, 24 warnings

100% 00:00:45